

Name: Pranjal Verma, B. Tech (EE), IC-ResQ Lab.


Work Completed –

1. Schematic to GDS-II: (complete flow)


- Schematic of Inverter
- Symbol
- Testbench
- Pre-simulation – Dynamic power, Leakage power and Transient response.
- Layout
- DRC
- LVS
- QRC
- Post Layout Simulation
- Pad Frame (Schematic, Layout and DRC)
- Stream-out GDS -II

Inverter


Schematic

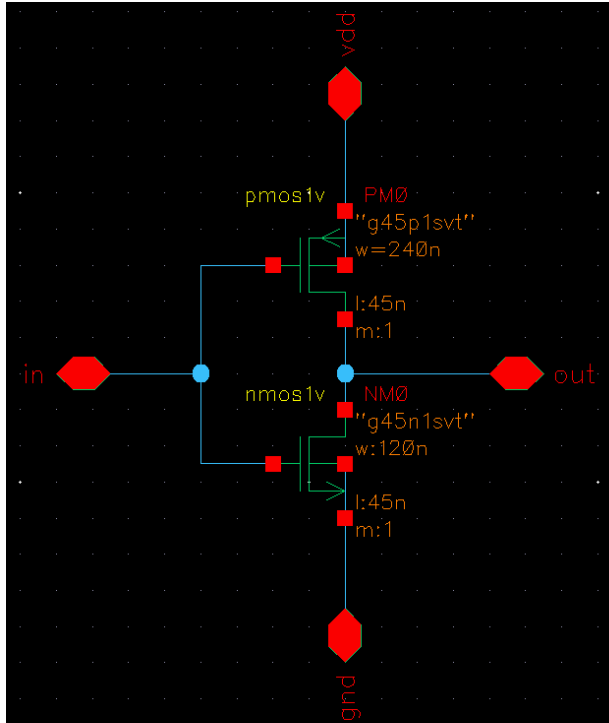


Symbol

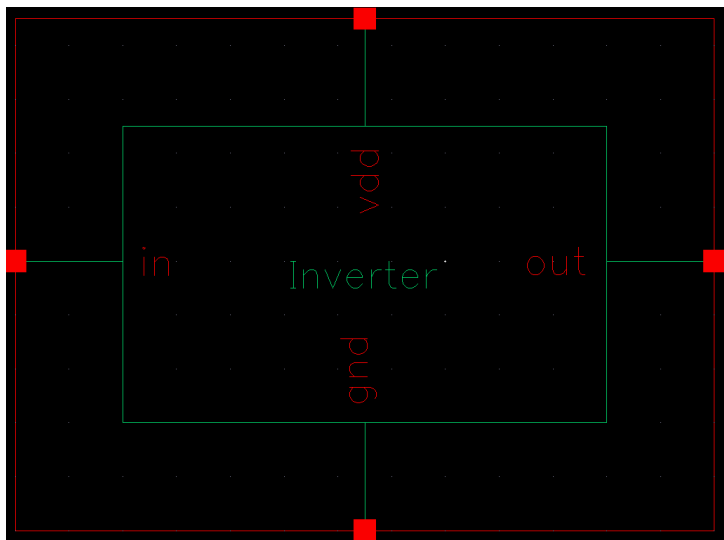


Testbench:

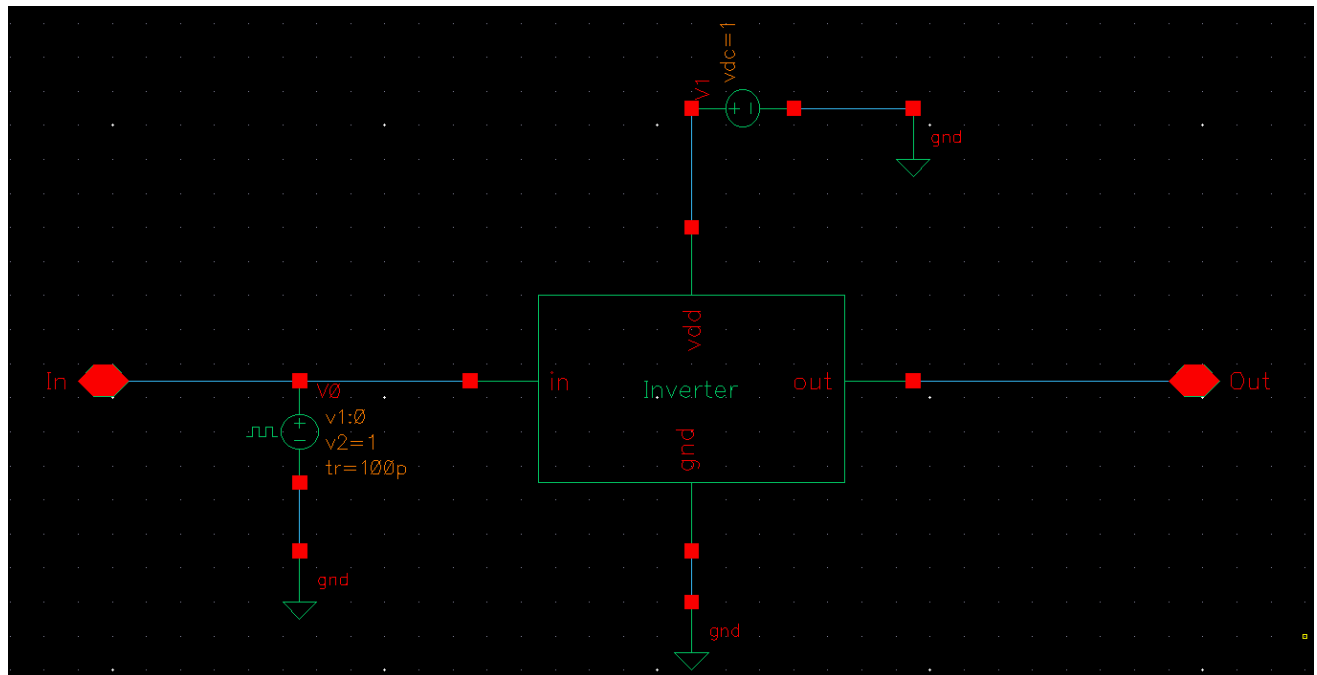


Transient Response:

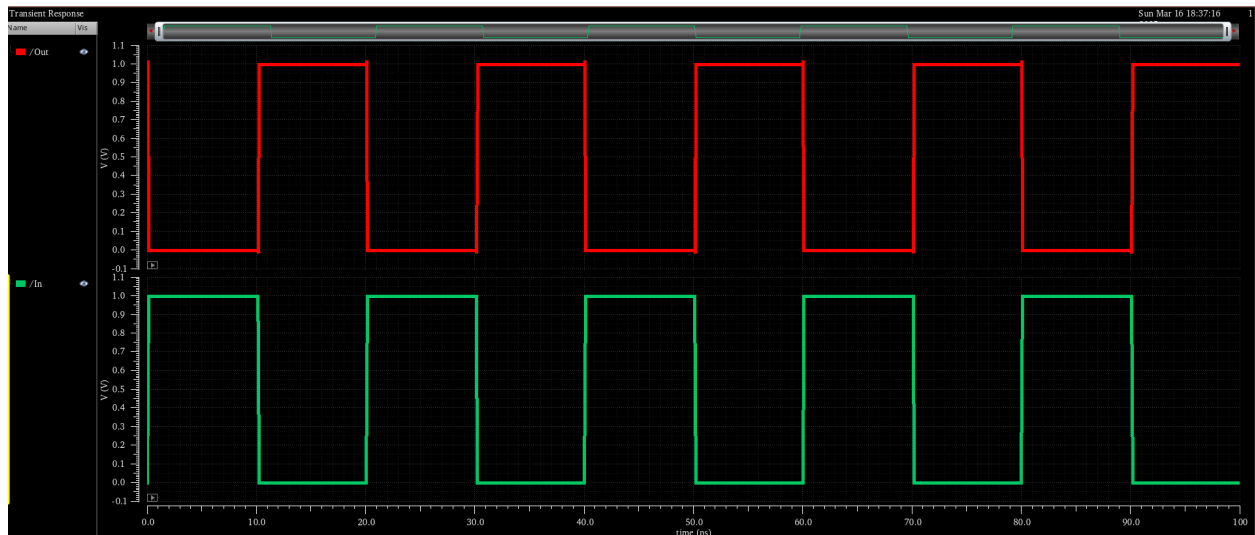


Dynamic power and propagation:

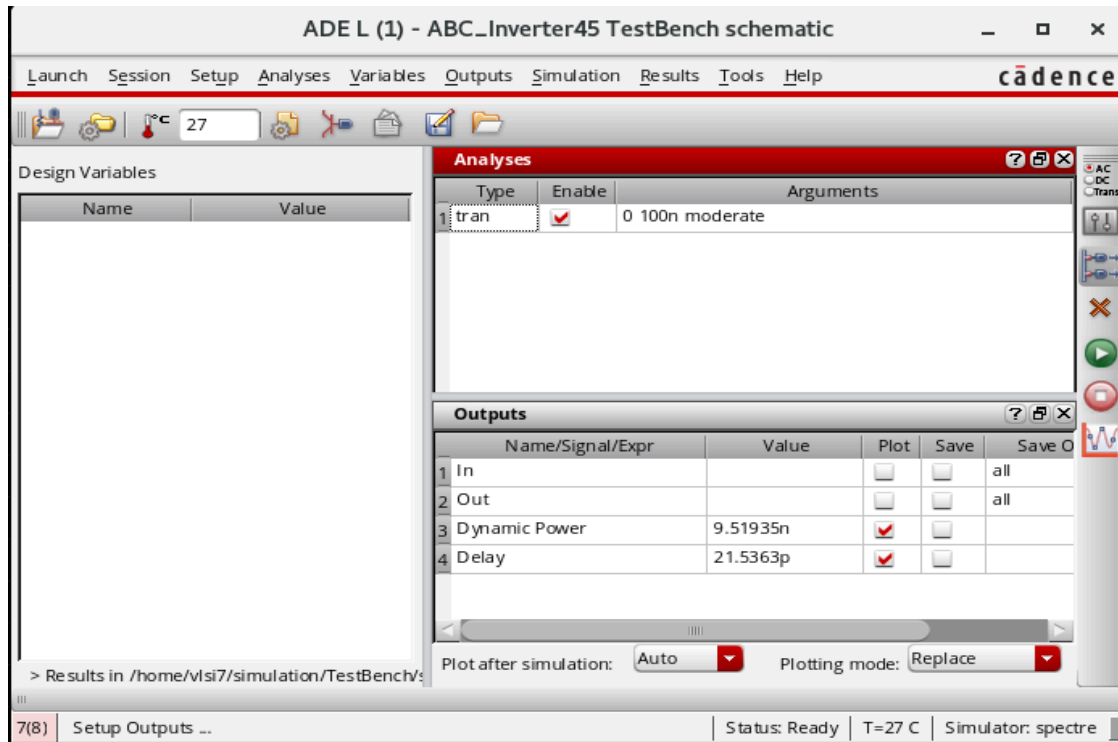


Layout :

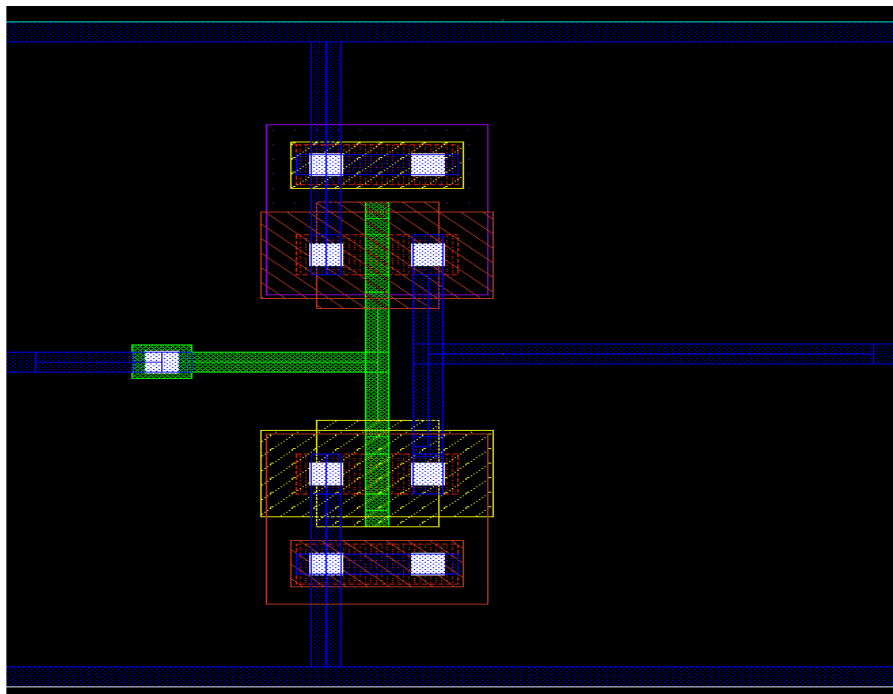


DRC :

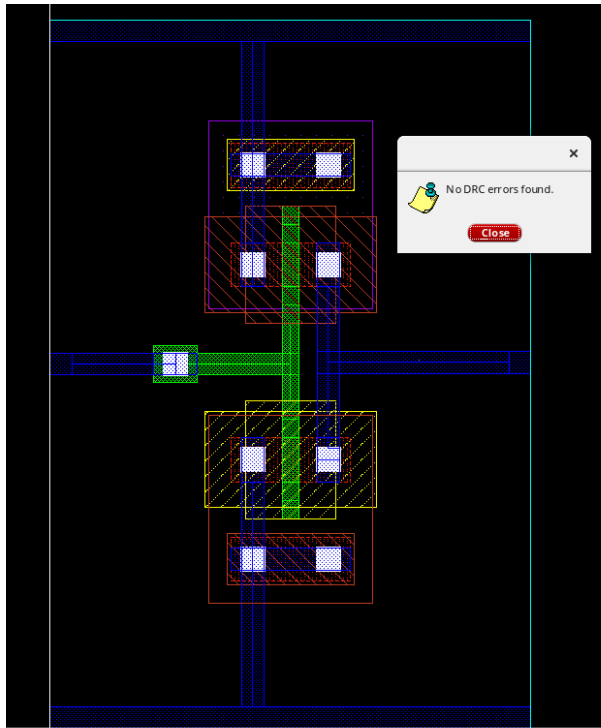


LVS:

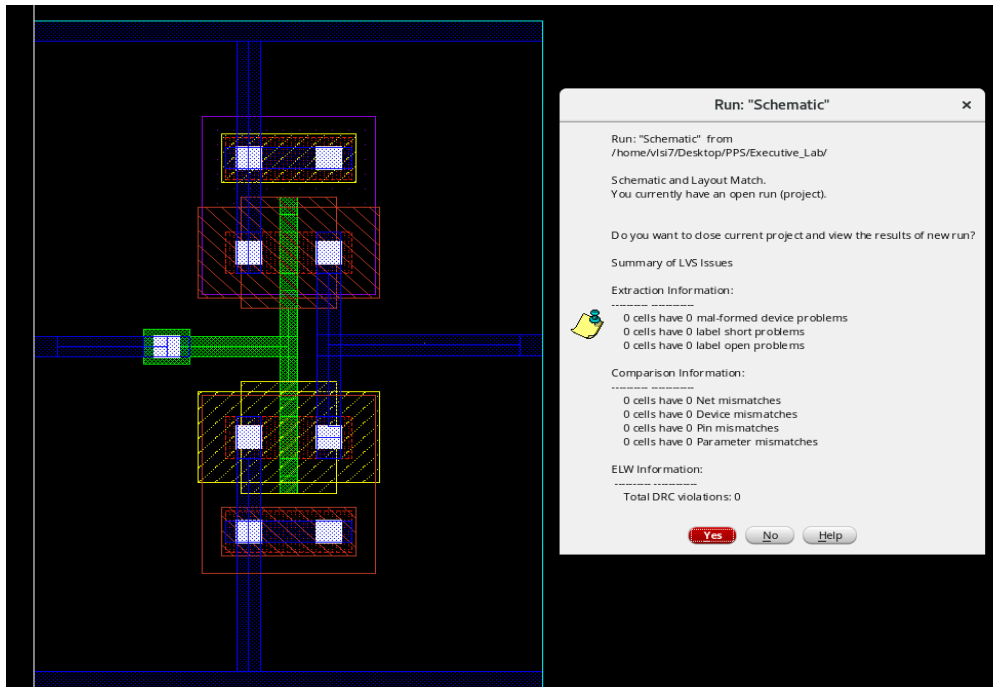

QRC:

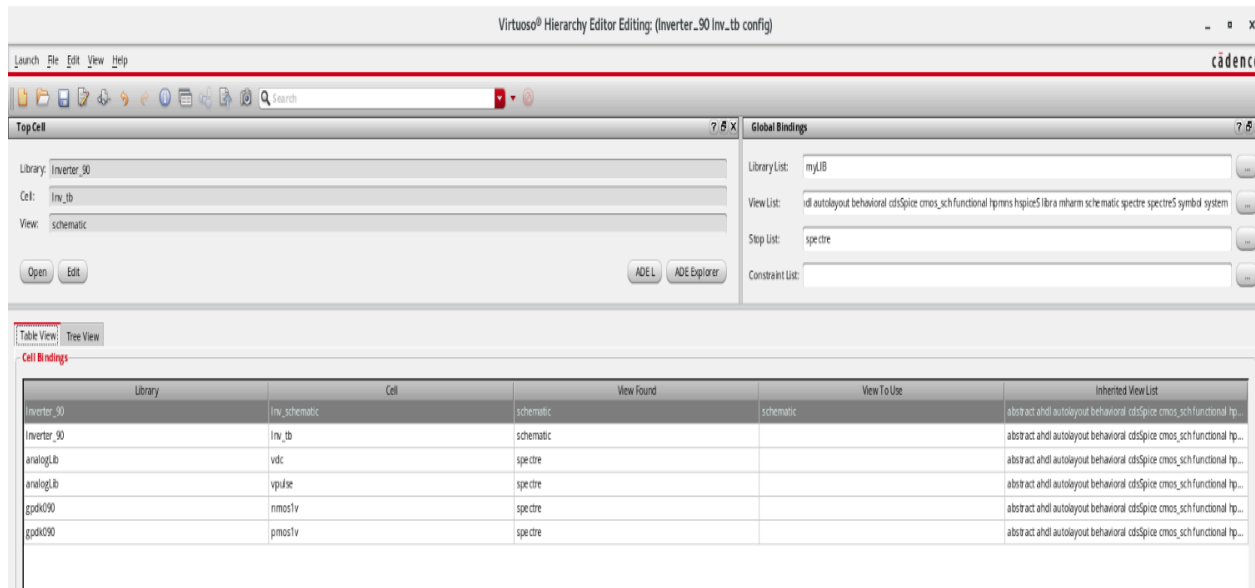

AV-extracted view -

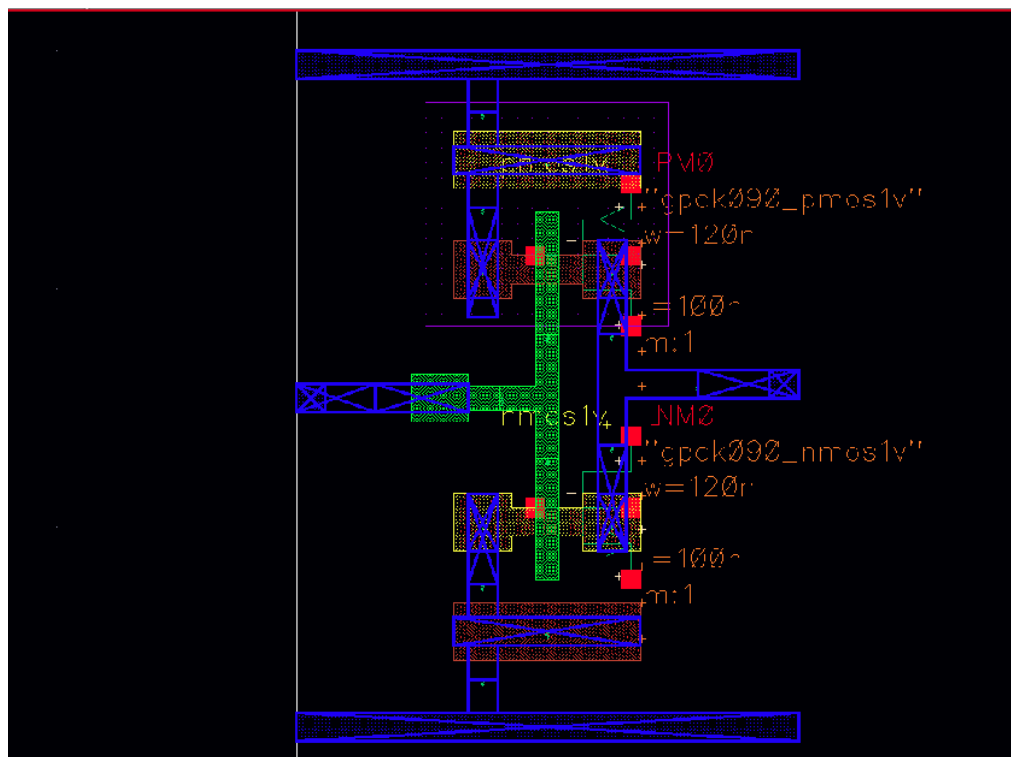


Post Layout Simulation:



Pad Frame :

Schematic :

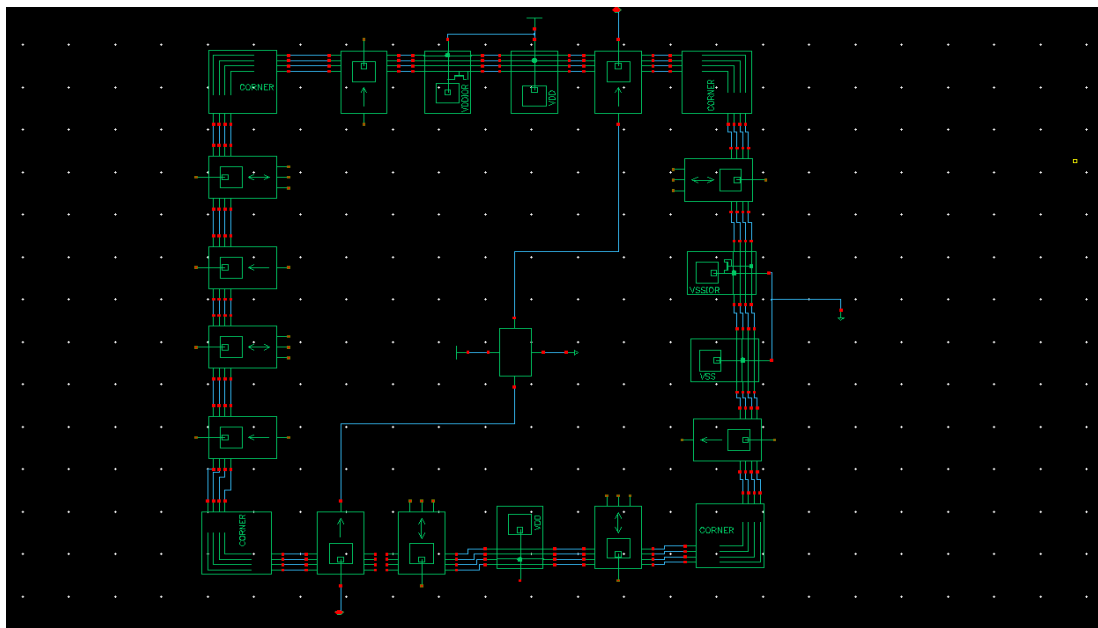

Layout:

